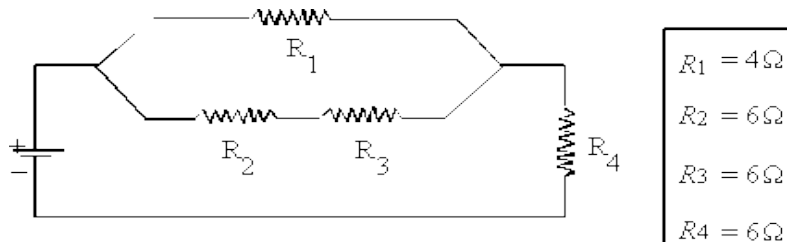


Electrical circuits exercises

Exercises collection obtained from: <http://laurenhill.emsb.qc.ca/science/ansp32.html>

1. An electric circuit is illustrated below:



What is the equivalent resistance of this circuit?

$$R_2 + R_3 = R_{eq}$$

$$6 + 6 = 12 \Omega$$


$$1/R_p = 1/R_1 + 1/R_{eq}$$

$$1/R_p = 1/4 + 1/12$$

$$R_p = 3 \Omega$$

$$R_t = R_{eq} + R_p = 3 + 6 = 9 \Omega$$

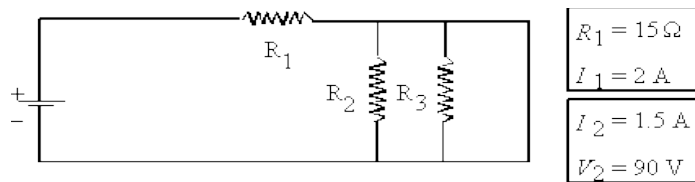2. An electric circuit is illustrated below.



What is the value of resistor R3?

$$I_1 = I_2 + I_3 \text{ because } I_1 \text{ is the total current in this case.}$$

$$2 = 1.5 + I_3$$


$$I_3 = 0.5 \text{ A}$$

$$\text{If } V_2 = 90 \text{ V, then } V_3 = 90 \text{ V because voltage is the same in parallel connection.}$$

$$R_3 = V_3/I_3 = 90/0.5 = 180 \Omega$$

3. Given this electric circuit:

Find the equivalent resistance, R_t .

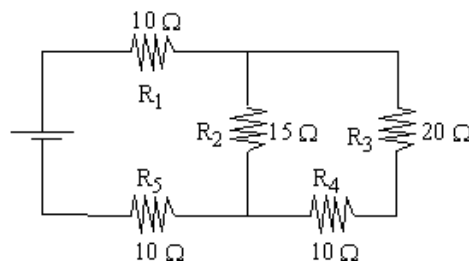

$$R_4 \text{ and } R_3 \text{ are in series so } R_{eq1} = R_4 + R_3 = 10 + 20 = 30\Omega$$

R_2 and R_{eq1} are in a parallel connection, so:


$$1/R_{eq2} = 1/R_2 + 1/R_{eq1}$$

$$1/R_{eq2} = 1/15 + 1/30$$

$$R_{eq2} = 10 \Omega$$

$$R_t = R_5 + R_{eq2} + R_1 = 10 + 10 + 10 = 30 \Omega$$

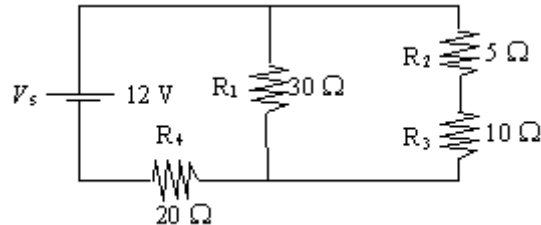4. A series-parallel electric circuit is illustrated below:



What is the voltage value across the terminals of resistor R_1 ?

First find total resistance:

$$1/R_{eq} = 1/R_1 + 1/(R_2 + R_3)$$

$$1/R_{eq} = 1/30 + 1/(5 + 10) = 1/30 + 1/15 = 1/30 + 2/30 = 3/30 = 1/10$$

$$R_{eq} = 10 \Omega$$


$$R_t = R_4 + R_{eq} = 20 + 10 = 30 \Omega$$

$$I_t = V/R = 12/30 = 0.40 \text{ A}$$

$$V_4 = IR_4 = 0.40 \times 20 = 8 \text{ V}$$

$$V_1 = V_t - V_4 = 12 - 8 = 4 \text{ V}$$

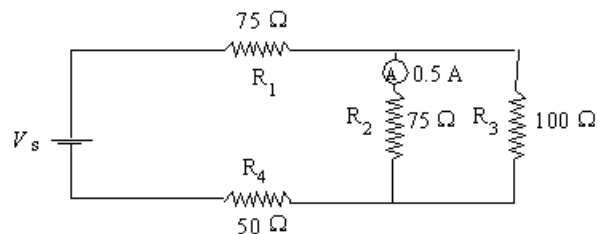5. A series-parallel electric is illustrated below.




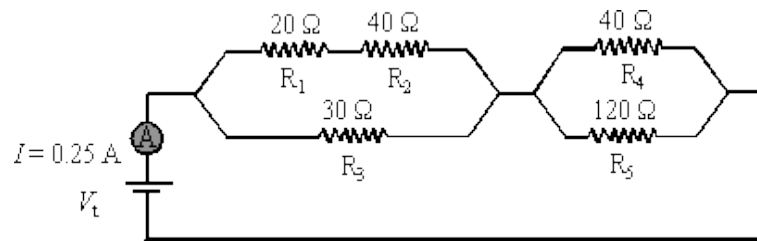
What is the intensity of the current flowing through the power source, I_s ?

R_2 and R_3 experience the same voltage, so $V_2 = I_2 R_2 = (0.5)75 = 37.5 \text{ V}$ and:

$$I_3 = V_3/R_3 = 37.5/100 = 0.375 \text{ A}$$

$$\text{So total current} = 0.5 + 0.375 = 0.875 \text{ A}$$

6. The following electric circuit consists of a power supply, five resistors (R_1 , R_2 , R_3 , R_4 and R_5) and an ammeter  (An ammeter is a device used to measure the current value at a specific point in an electrical circuit.).



The ammeter reads 0.25 A.

- a) What is the voltage (V_t) across the terminals of the power supply?

$$1/R_{eq1} = 1/(R_1 + R_2) + 1/R_3$$

$$1/R_{eq1} = 1/(20 + 40) + 1/30$$

$$R_{eq1} = 20 \Omega$$

$$1/R_{eq2} = 1/R_4 + 1/R_5$$

$$1/R_{eq2} = 1/40 + 1/120$$

$$R_{eq2} = 30 \Omega$$

$$R_t = R_{eq1} + R_{eq2} = 20 + 30 = 50 \Omega$$

$$V_t = IR_t = 0.25 \times 50 = 12.5 \text{ V}$$

- b) What is the voltage across R_3 ?

$$V_p = V_3 = I_t R_{eq1} = 0.25 \times 20 = 5 \text{ V}$$

- c) What is the potential difference across R_1 ?

$$I_1 = V_p/(R_1 + R_2) = 5/(20 + 40) = 0.0833 \text{ A}$$


$$V_1 = I_1 R_1 = 0.0833 \times 20 = 1.67 \text{ V}$$

- d) What current flows through R_5 ?

$$V_5 = V_t - V_3 = 12.5 - 5 = 7.5 \text{ V}$$

$$I_5 = V_5/R_5 = 7.5/120 = 0.0625 \text{ A}$$

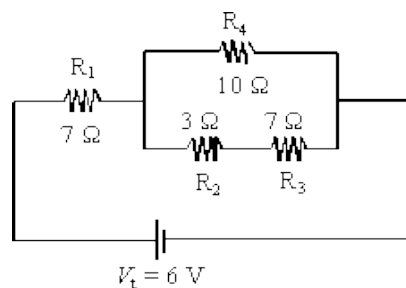7. An electric circuit is illustrated below:



What is the value for the current flowing through resistors R_2 and R_3 ?

$$R_{eq} = 1/R_4 + 1/(R_2 + R_3)$$

$$R_{eq} = 1/10 + 1/(3 + 7)$$


$$R_{eq} = 5 \Omega$$

$$R_t = R_1 + R_{eq} = 7 + 5 = 12 \Omega$$

$$I_t = V_t/R_t = 6/12 = 0.5 \text{ A}$$

Current flowing through R_2 and R_3 will be the same as what's on top (since R is the same), so it will be $0.5/2 = 0.25 \text{ A}$

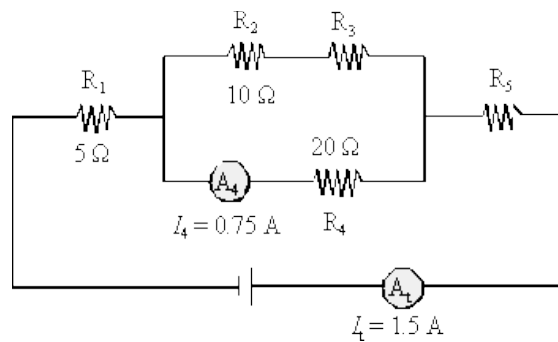8. The following electric circuit consists of a power source, five resistors (R_1, R_2, R_3, R_4 and R_5) and two ammeters A_4 and A_t .



What is the voltage value across the terminals of resistor R_3 ?

R_2 and R_3 are receiving the same current (they are in series connection) and its value is $1.5 - 0.75 = 0.75 \text{ A}$ (the difference between A_t and A_4)


That means that current is the same in both branches. That implies that resistance has to be also the same in both branches ($R_2 + R_3 = R_4$).

$$\text{So } R_3 = 20 - 10 = 10 \Omega$$

Now in order to calculate the voltage value across R_3 :

$$V_3 = I_3 R_3 = 0,75 \times 10 = 7,5 \text{ V}$$

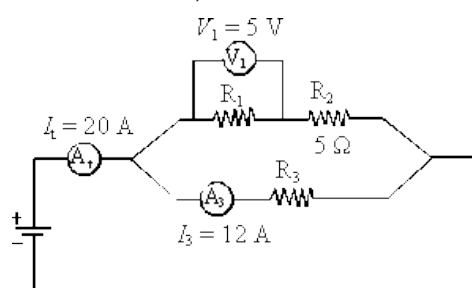9. The following circuit consists of a power source, two ammeters A_1 and A_3 , a voltmeter V_1 and three resistors (R_1, R_2 and R_3). (A voltmeter is a device used to measure voltage across two points in an electrical circuit).



Total current I_t is 20 A, I_3 is 12 A. Voltage V_1 across the terminals of resistor R_1 is 5 V.

What is the resistance of resistor R_3 ?

$$I_1 = I_t - I_3 = 20 - 12 = 8 \text{ A} = I_2$$


$$V_2 = I_2 R_2 = 8 \times 5 = 40 \text{ V}$$

$$V_1 + V_2 = V_3$$

$$5 + 40 = V_3 = 45 \text{ V}$$

$$R_3 = V_3/I_3 = 45/12 = 3.75 \text{ } \Omega$$

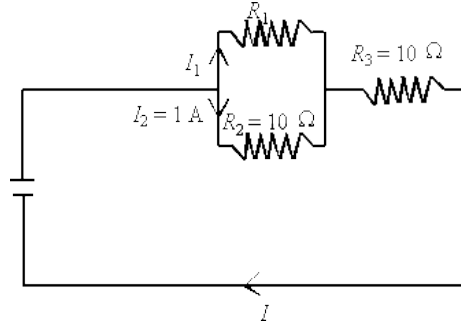10. A power source with a voltage of 30 V is connected to the circuit shown below.



What is the current I across the circuit?

$$V_2 = I_2 R_2 = 1 \times 10 = 10 \text{ V}$$


$$V_3 = V_t - V_2 = 30 - 10 = 20 \text{ V}$$

$$I_t = V_3/R_3 = 20/10 = 2$$


11. How can one 25 Ω and two 100 Ω resistors be connected so that their total resistance is 75 Ω ?

Place the two 100 Ω resistors in parallel (so $R_{eq} = 50 \Omega$) and put the new branch in series with the 25 Ω .

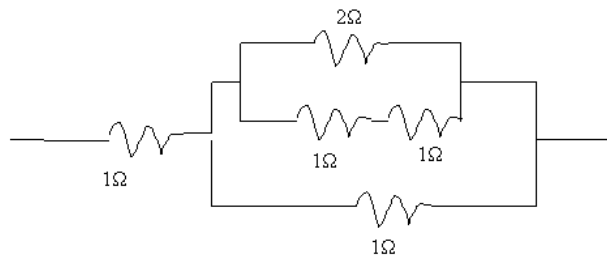12. How can four 1.0 Ω resistors and one 2.0 Ω resistor be connected to give a combined resistance of 1.5 Ω ?



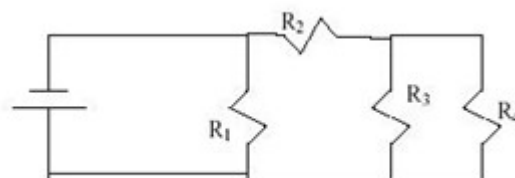13. Four identical resistors are connected as shown. If the total voltage is 12V, find the voltage across each resistor:



R_1 has the full 12V because it is just connected in series with only the battery.

R_2 has twice the resistance of R_3 and R_4 combined (because R_3 and R_4 are in a parallel connection), so it will have twice the voltage. $12 = 2x + x$; $x = 4 \text{ V}$.

Conclusion $V_2 = 2x = 8\text{V}$; V_3 and $V_4 = 4\text{V}$